

# Simple Line-Following Robot



AJINKYA D. DIXIT

Generally, line-follower robots are microcontroller-based. Here we describe a line-follower robot without microcontroller

TCRT5000L reflective optical sensors (IC1 and IC2), inverter 74LS04 (IC3), motor driver L293D (IC4), regulator 7805 (IC5) and a few discrete components.

TCRT5000L optical sensors are

L293D is a quadruple high-current, half-H driver. It is designed to provide bidirectional drive current of up to 600 mA at 4.5V to 36V. The device is designed to drive inductive loads such as motors as well as other high-current/high-voltage loads in positive-supply applications.

The motor drivers are enabled in pairs. When enable input pins 1 and 9 of IC4 are high, the associated drivers for M1 and M2 are enabled and their outputs pin 3 and 6, and pins 11 and 14, respectively, are active and in phase with the inputs.

With the proper data inputs, each pair of drivers forms an H-bridge reversible drive suitable for motor applications. Motors M1 and M2 rotate in forward direction (say clockwise) when both the sensor outputs are low.

If you want the robot to follow a black track (made using black-colour tape) on a white floor, you need to connect jumpers SJ1 and SJ2 to B terminals as shown in Fig. 1. The robot will move as follows: When the left sensor, say IC2, detects the black track, the robot turns right. When the right sensor, say, IC1, detects the black track, the robot turns left. When both the sensors are in white surface then, the robot moves in forward direction.

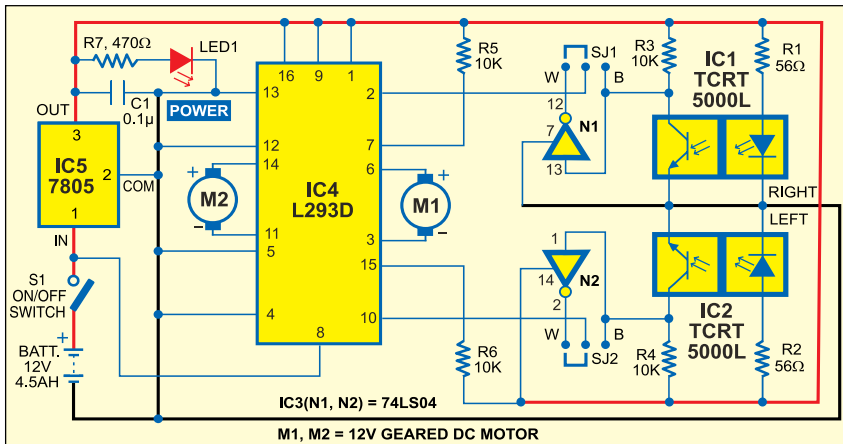


Fig. 1: Circuit of the line-following robot

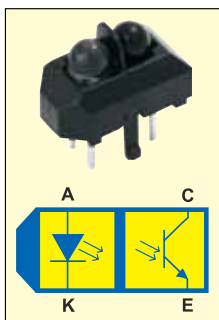


Fig. 2: Sensor and its internal details

for those who are not familiar with microcontrollers. It is a simple project, which can be taken up as a classroom assignment. It lays the foundation for building your own behaviour-based

(simulated) robot. The robot uses interfaces for the sensors to make the behaviour of the robot as versatile as possible. Two light detectors are mounted at the front of the robot. Also, a path is provided for the robot to follow—either a black track (using black colour tape) on a white floor or a white track on a black floor.

## Circuit description

Fig. 1 shows the circuit of the line-following robot. It comprises two

used as line-detecting sensors. The TCRT5000L reflective sensor includes an infrared emitter and photo-transistor in a leaded package. The sensor and its internal details are shown in Fig. 2.

When an object comes in the sensing area, the emitted IR light reflects off the object back to the photo-transistor. So the amount of light energy reaching the detector increases. This change in light energy or photo-current is used as the input signal to activate the motors of the line-follower robot.

The collector current of the photo-transistor is also dependent on the distance of the object's reflector surface from the sensor. The intensity of the reflected signal returning to the detector depends on the surface over which the robot moves. White surface reflects maximum infrared signal, while black surface absorbs maximum infrared signal.

Motor driver L293D is interfaced with sensors and controls the 12V geared DC motors M1 and M2. The

## PARTS LIST

### Semiconductors:

IC1, IC2	- TCRT5000L reflector module
IC3	- 74LS04 hex inverter
IC4	- L293D motor driver
IC5	- 7805, 5V regulator
LED1	- 5mm LED
DIS1-DIS5	- LTS543, CC7 segment display

### Resistors (all 1/4-watt, ±5% carbon):

R1, R2	- 56-ohm
R3-R6	- 10-kilo-ohm
R7	- 470-ohm
R8-R29	- 330-ohm

### Capacitors:

C1	- 0.1μF ceramic disk
----	----------------------

### Miscellaneous:

M1, M2	- 25-rpm geared DC motor
BATT.	- 12V, 4.5Ah battery
S1, S2	- On/off switch

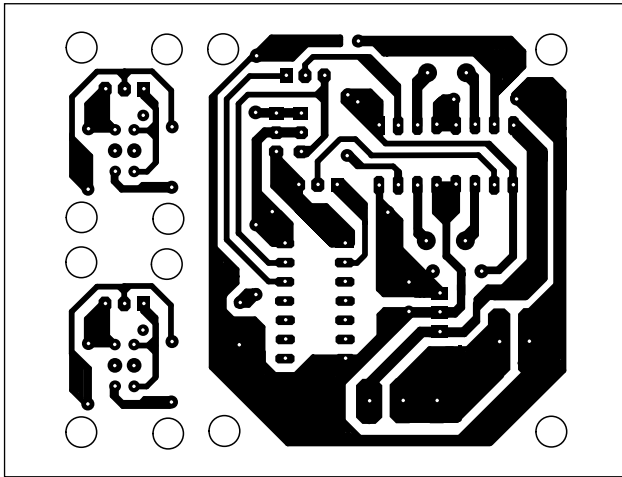


Fig. 3: An actual-size, single-side PCB for the line-follower robot

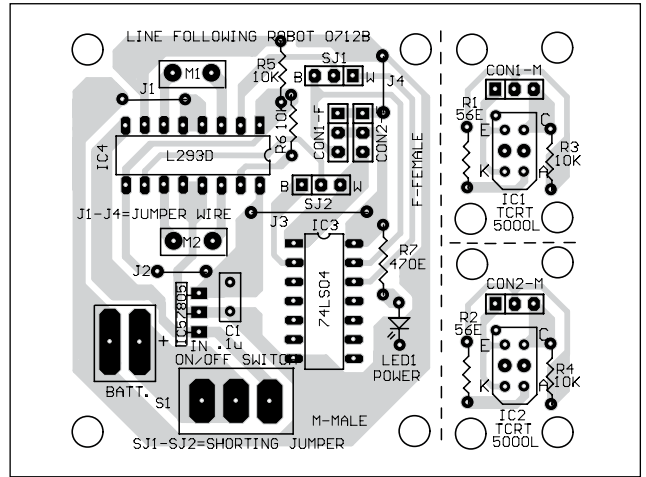


Fig. 4: Component layout for the PCB of Fig. 3

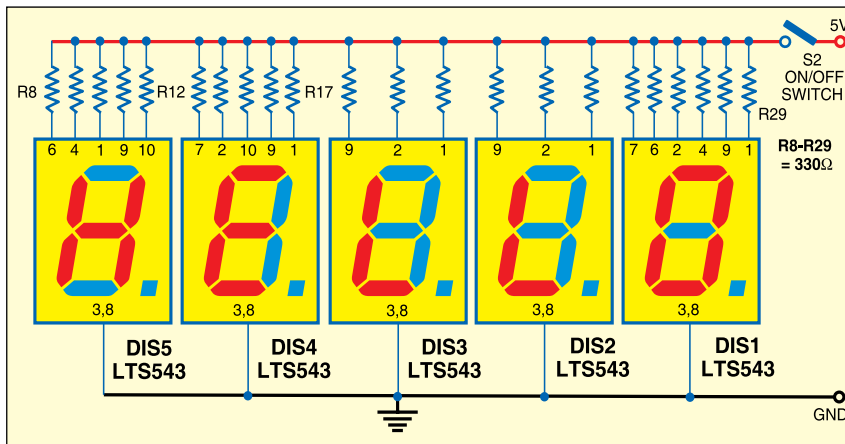


Fig. 5: Circuit for HELLO

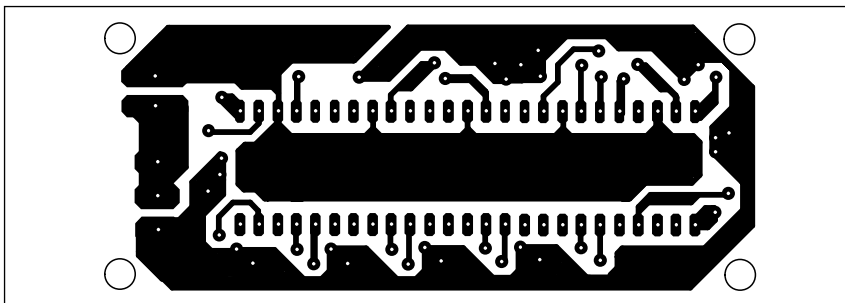


Fig. 6: An actual-size, single-side PCB for Fig. 5

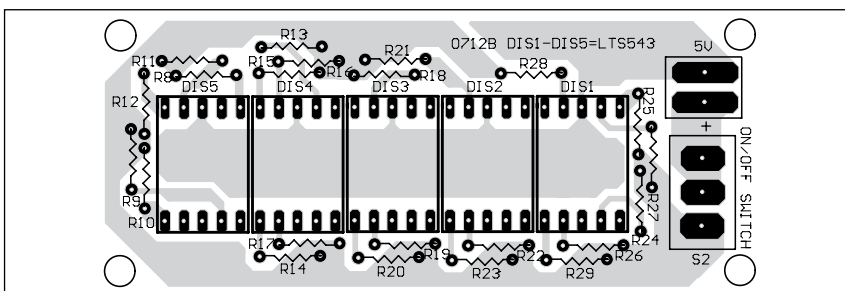


Fig. 7: Component layout for Fig. 6

If you want the robot to follow a white track change the jumpers' positions towards W terminals. As the reflector sensor moves on the black surface, the emitted signals are absorbed by the black surface and both the inverters (N1 and N2) invert to low. These low signals are fed to the motor driver L293D and the robot moves forward. When the left sensor, say IC2, detects the white track, the robot turn right. When right sensor, say IC1, detects the white track, the robot turns left. When both the sensors are in black surface then the robot moves in forward direction.

The circuit is powered by a 12V DC battery. IC 7805 is used to provide regulated 5V supply to the circuit. Capacitor C1 bypasses the ripples from the regulated supply. LED1 acts as the power-'on' indicator and resistor R7 limits the current through LED1.

### Construction and testing

An actual-size, single-side PCB for the line-follower robot is shown in Fig. 3 and its component layout in Fig. 4.

The sensors sections should be separated from the main PCB by cutting along the dotted lines. Right and left sensors should be mounted on the front of the robot with both the sensors facing towards the ground. Distance between the right and left sensors should be aligned properly as per the width of the track on the ground.

Assemble the circuit on a PCB as it

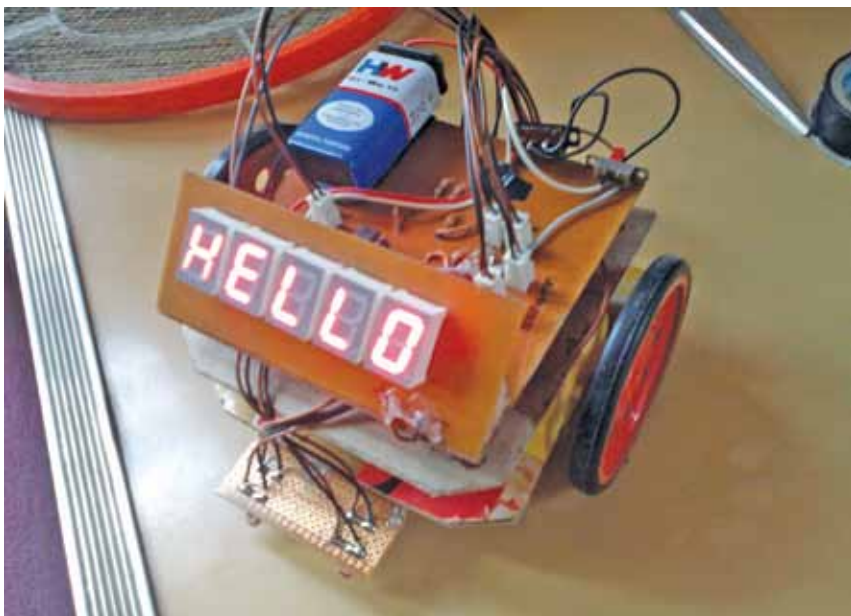


Fig. 8: Author's prototype

minimises time and assembly errors. Carefully assemble the components and double-check for any overlooked error. Use of IC bases for IC3 and IC4 is recommended. Before putting the ICs, always check the correct supply voltage. Suitable connectors are provided on the PCB to connect geared motors M1 and M2 and sensors IC1 and IC2. Connect the motors and power the circuit with a 12V battery. Place the robot on the track. Sensors sense the white or black track on the surface and the robot follows that track. To decorate the line follower robot by using HELLO on the top. Circuit diagram for HELLO is given in Fig. 5. An actual-size, single-side PCB for Fig. 5 is shown in Fig. 6 and its component layout in Fig. 7. Working prototype photograph is given in Fig. 8

---

*The author is a BE final-year student of information technology. His interests include electronics and robotics, website designing, software development and microcontrollers*