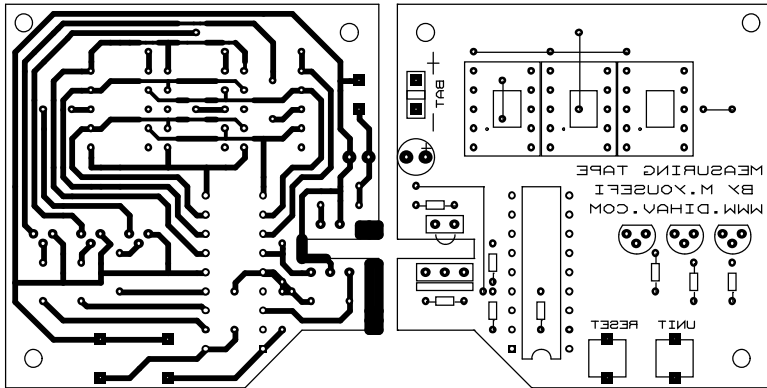


## Digital Measuring Tape

By Mohammad Yousefi (vahid\_you2004@yahoo.com)

www.dihav.com



Print this page on an **A5 glossy paper** with a **laser printer without scaling**.

Microcontroller is a PIC16F819

All transistors are BC547

Capacitor is a 100 $\mu$ F electrolyte capacitor

The resistor behind IR transmitter is a 470 $\Omega$  resistor and all other resistors are 10k $\Omega$

7 segments are common anode