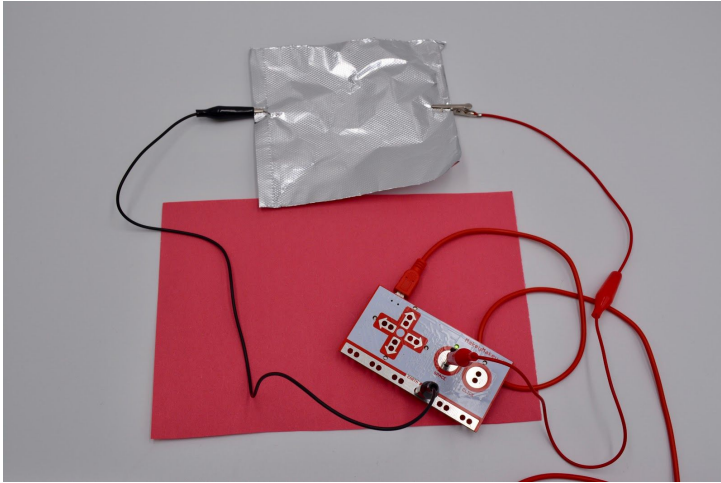



Step One:

Hook Makey Makey to a piece of foil as pictured.
This completes a circuit.




Step Two:

Tear the foil and break the circuit!

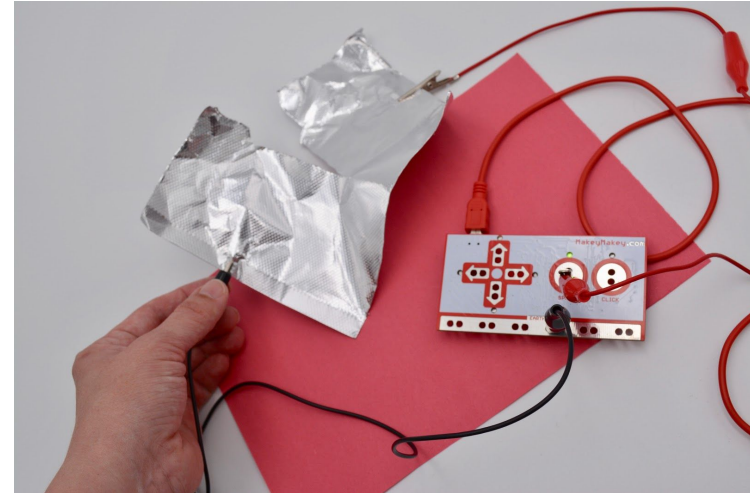


Step Three:


The circuit is broken and incomplete.

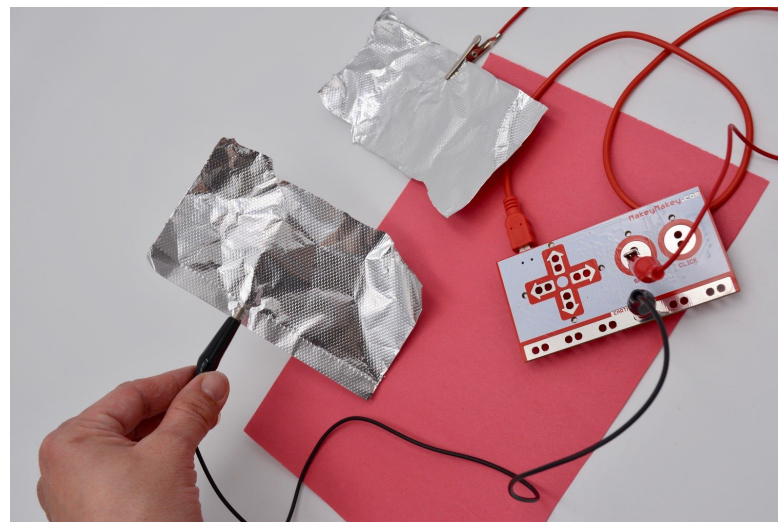

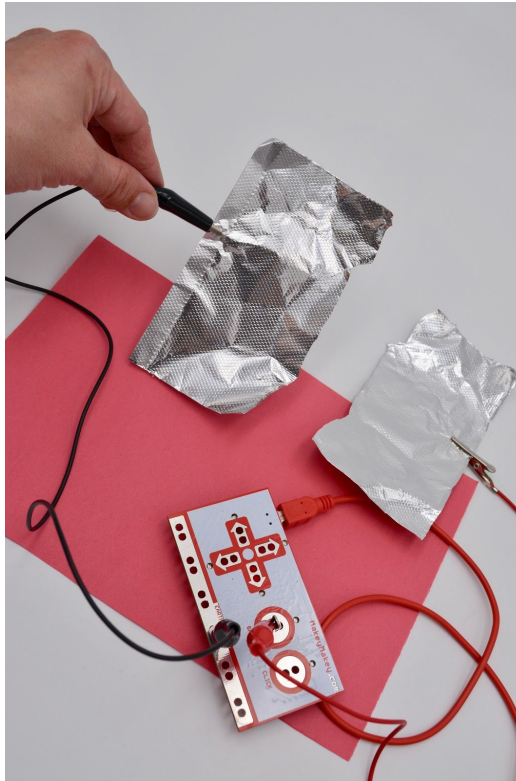Incomplete Circuit: Electrons cannot flow...



Complete Circuit: Electrons are flowing!

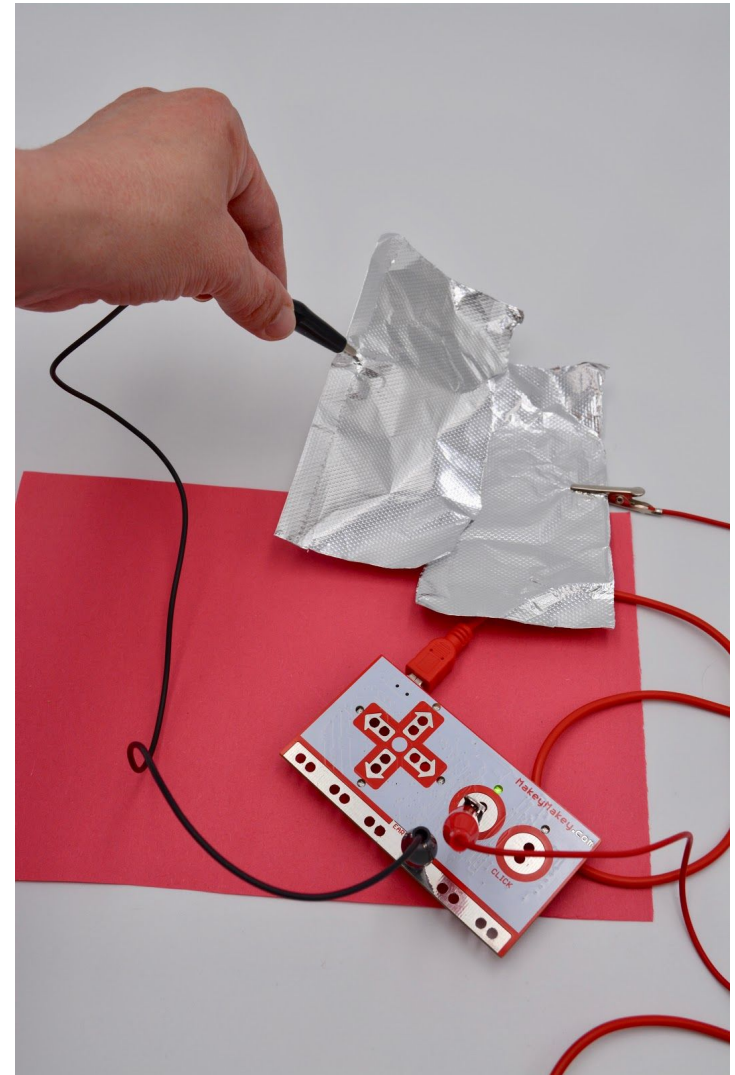

Step Four:

Turn your experiment into a switch! This is the same science behind lightswitch at home!

