


All references in this writeup are to the Atmel ATtiny2313/V Preliminary Reference Manual.

## 1 Choosing the LED current limiting resistor

At most two LEDs are on at any time and, by design, the duty cycle is at most 20%. There are two main constraints; (1) the maximum DC pin current must be  $\leq 40\text{mA}$ , and (2) the total high pin current must be  $\leq 60\text{mA}$ . (It's not entirely clear if the latter constraint is a DC or transient constraint, we will treat it as transient, which is more stringent.)

The CR2032 batteries have a typical internal resistance of  $20\Omega$ , hence the supply resistance is  $40\Omega$ . Fig. 105 suggests that the driving pin resistance is about  $25\Omega$ .

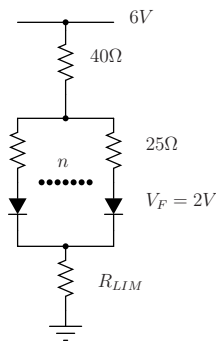The total LED current required to drive  $n$  LEDs simultaneously can be estimated using the following equivalent circuit:



The transient constraint gives:

$$\frac{6 - 2}{40 + \frac{25}{n} + R_{LIM}} \leq 60 \text{ mA} \quad (1)$$

or, equivalently:

$$R_{LIM} \geq 26.6 - \frac{25}{n} \Omega \quad (2)$$

Letting  $n = 2$  gives the worst case (by design), which is  $R_{LIM} \geq 14.16\Omega$ . The nearest value I have in my box is  $R_{LIM} = 10\Omega$ , which should be fine. The estimate above gives a total LED current of  $53\text{mA}$  if one LED was lit, and  $64\text{mA}$  if two LEDs were lit. The DC constraint is easily satisfied since the maximum DC current *per pin* is  $\leq (0.2)64 = 12.8\text{mA}$  (since the duty cycle is at most 20%).

The  $64\text{mA}$  is slightly higher than the total pin current constraint, which is fine in this context, but just for giggles, a better estimate can be made by using a load-line analysis. (A  $60\text{mA}$  supply current will result in a significant drop because the CR2032 internal resistance is fairly high.) Fig. 105 on p.196 gives the driving point I-V characteristic for a pin driven high. This characteristic can be nicely modeled by a quadratic, and the LED modelled as a drop of  $V_F$ . Superimposing the lines in Fig. 1 shows that the above estimate was generous, the total LED current based on a load-line analysis is  $40\text{mA}$  if one LED was lit, and  $48\text{mA}$  (twice the single LED current) if two LEDs were lit.


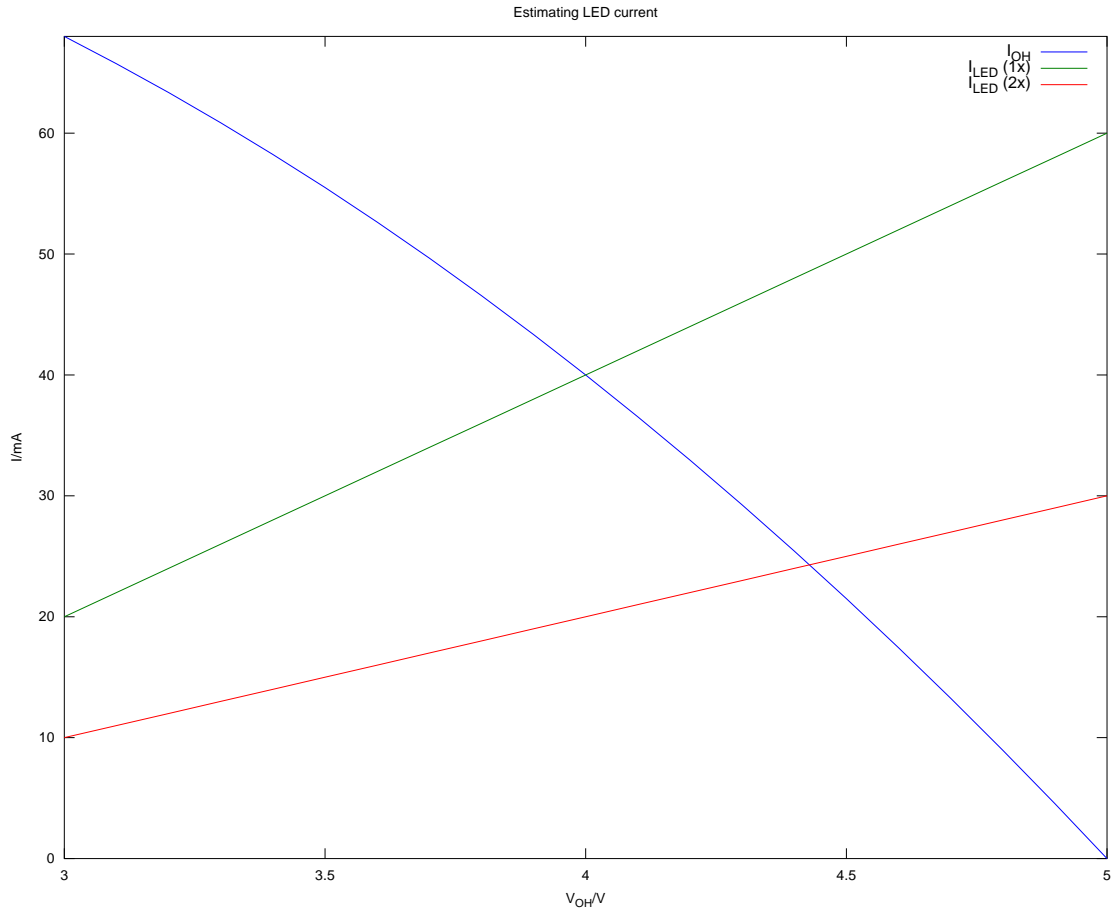


Figure 1: LED current estimation.

I should be careful to point out that the above load-line analysis is still very rough, as it assumes that the driving point characteristic of the pin is unaffected by the supply voltage (which is affected by the current draw). A quick look at the specs. shows that this is not true, however the driving point characteristics for lower supplies result in a lower current, so this is still a slightly conservative estimate.

In fact, a load-line analysis shows that removing  $R_{LIM}$  entirely would also remain under the 60mA constraint. However, I figured this out after I had built the circuit!
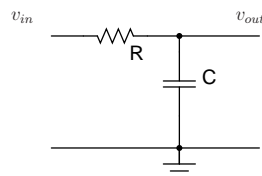
## 2 Analysing the RC charge/discharge circuit



For a reasonable input voltage  $v_{in}(\cdot)$ , the output voltage  $v_{out}(\cdot)$  of the  $RC$  circuit is given by the formula:

$$v_{out}(t) = v_{out}(0)e^{-\frac{t}{RC}} + \frac{1}{RC} \int_0^t e^{-\frac{t-\tau}{RC}} v_{in}(\tau) d\tau \quad (3)$$

If the input voltage is a constant  $V_{in}$ , then this can be simplified to:

$$v_{out}(t) = v_{out}(0)e^{-\frac{t}{RC}} + V_{in}(1 - e^{-\frac{t}{RC}}) \quad (4)$$

There are two cases of interest to us; charging and discharging. In the case of charging,  $v_{out}(0) = 0$  (assuming the low output,  $V_{OL} = 0$ ), and  $V_{in} = V_{OH}$ , which gives:

$$v_{out}(t) = V_{OH}(1 - e^{-\frac{t}{RC}}) \quad (5)$$

In the discharging case, we take  $v_{out}(0) = V_{OH}$ , and  $V_{in} = 0$ , giving:

$$v_{out}(t) = V_{OH}e^{-\frac{t}{RC}}. \quad (6)$$

In the above, I use  $V_{OH}$  rather than  $V_{CC}$  as the high voltage, mainly as a reminder that the coin cell IR drop is fairly large, so  $V_{OH}$  and  $V_{CC}$  can differ by more than usual.

### 3 Choosing $R_{DIS}$

The capacitor should be discharged as quickly as possible, the limitations are that the maximum DC pin current must be  $\leq 40\text{mA}$ , and the maximum transient current must be  $\leq 60\text{mA}$ . During discharge the pin current is given by

$$i_{pin}(t) = \frac{V_{OH}}{R} e^{-\frac{t}{RC}}, \quad (7)$$

so the maximum current is  $\frac{V_{OH}}{R}$ , and the average discharge current can be computed by the following (in fact, this is an overestimate, since the discharges are not back to back), where  $k$  is the number of time constants over which the discharging occurs

$$\bar{i}_{pin} \leq \frac{1}{kRC} \int_0^{kRC} i_{pin}(\tau) d\tau \quad (8)$$

$$= \frac{1}{kRC} \frac{V_{OH}}{R} \int_0^{kRC} e^{-\frac{\tau}{RC}} d\tau \quad (9)$$

$$= \frac{V_{OH}}{R} \frac{(1 - e^{-k})}{k} \quad (10)$$

This shows that for  $k \geq 2$ ,  $\bar{i}_{pin} \leq \frac{1}{2} \frac{V_{OH}}{R}$ , and so the transient constraint is harder to satisfy than the DC constraint. To satisfy the transient constraint, we need

$$\frac{V_{OH}}{R} \leq 60\text{mA} \quad (11)$$

or, in terms of the resistance  $R$ ,

$$R \geq \frac{V_{OH}}{60\text{mA}} \quad (12)$$

Since  $V_{OH} \leq 6V$ , this results in  $R \geq 100\Omega$ .

## 4 Relationship of time to measured voltage

Formula 5 can be rewritten as

$$\frac{v_{out}(t)}{V_{OH}} = (1 - e^{-\frac{t}{RC}}) \quad (13)$$

The conversion time  $t_c$  is the time taken for  $v_{out}(t)$  to match the divided load resistor voltage  $v$ , hence

$$\frac{v}{V_{OH}} = (1 - e^{-\frac{t_c}{RC}}) \quad (14)$$

from which we get

$$t_c = RC \ln\left(\frac{1}{1 - \frac{v}{V_{OH}}}\right) \quad (15)$$

This can be used to (loosely) estimate the sensitivity of  $t_c$  to variations in  $V_{CC}$ . The divided load resistor voltage  $v$  is given by

$$v = \frac{22}{32}(V_{CC} - R_L i_d) \quad (16)$$

which gives

$$\frac{v}{V_{CC}} = \frac{22}{32}\left(1 - \frac{R_L i_d}{V_{CC}}\right) \quad (17)$$

So, abusing notation a little (and noting that in the saturation region  $i_d$  is roughly independent of  $V_{CC}$ ) we have

$$\frac{d\left(\frac{v}{V_{CC}}\right)}{dV_{CC}} = \frac{22}{32} \frac{R_L i_d}{V_{CC}^2} \quad (18)$$

Plugging in  $V_{CC} = 5V$ ,  $i_d = 9mA$  and  $R_L = 330\Omega$  shows that the sensitivity is less than  $0.03V^{-1}$ .

Assuming that changes in  $V_{OH}$  are the same as changes in  $V_{CC}$ , we can use Formula 15 to estimate the effect of changes in  $V_{CC}$  on  $t_c$ . Abusing notation again, we have

$$\frac{dt_c}{d\left(\frac{v}{V_{OH}}\right)} = RC \frac{1}{1 - \frac{v}{V_{OH}}} \quad (19)$$

By design, we have  $v \leq \frac{22}{32}V_{OH}$ , so we have

$$\frac{dt_c}{d\left(\frac{v}{V_{OH}}\right)} \leq 3.2RC \quad (20)$$

Plugging in  $RC = 470\mu S$  gives  $\frac{dt_c}{d\left(\frac{v}{V_{OH}}\right)} \leq 1504$ , from which we can estimate that the impact of the supply voltage change on the conversion time is about  $45\mu S/V$ , which is significant, but not a huge issue for this application.