

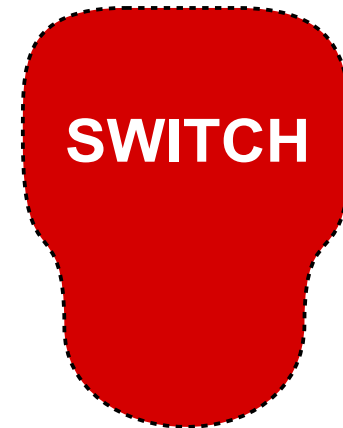
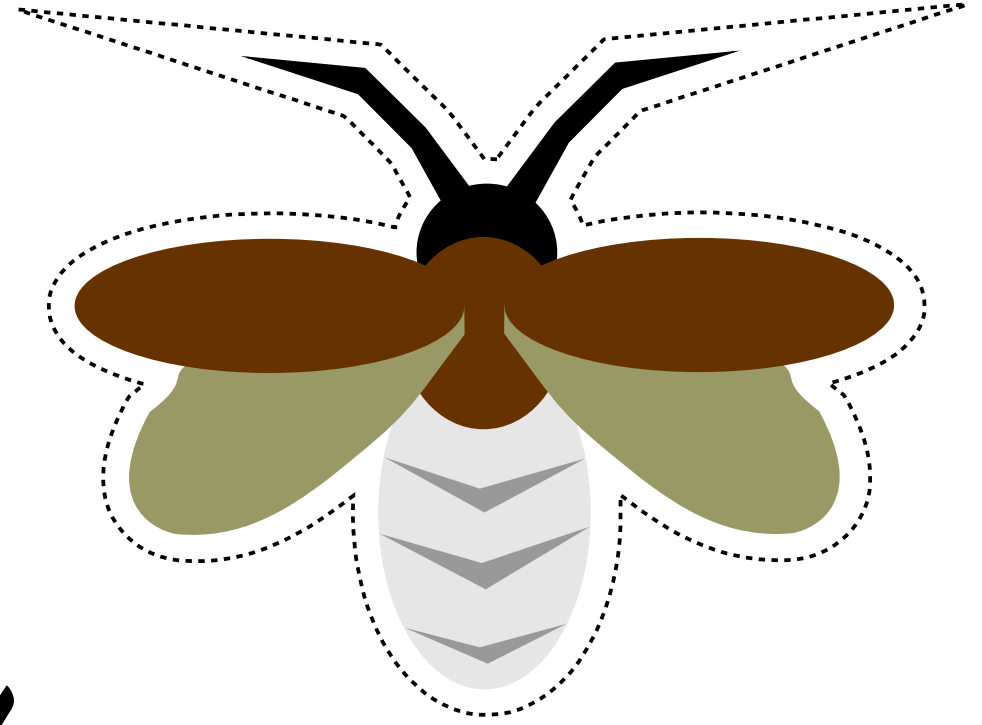
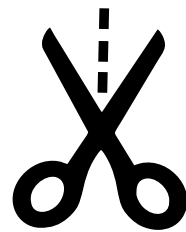
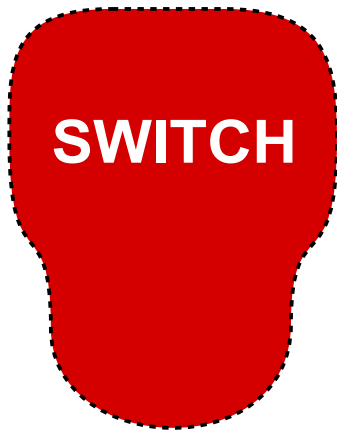
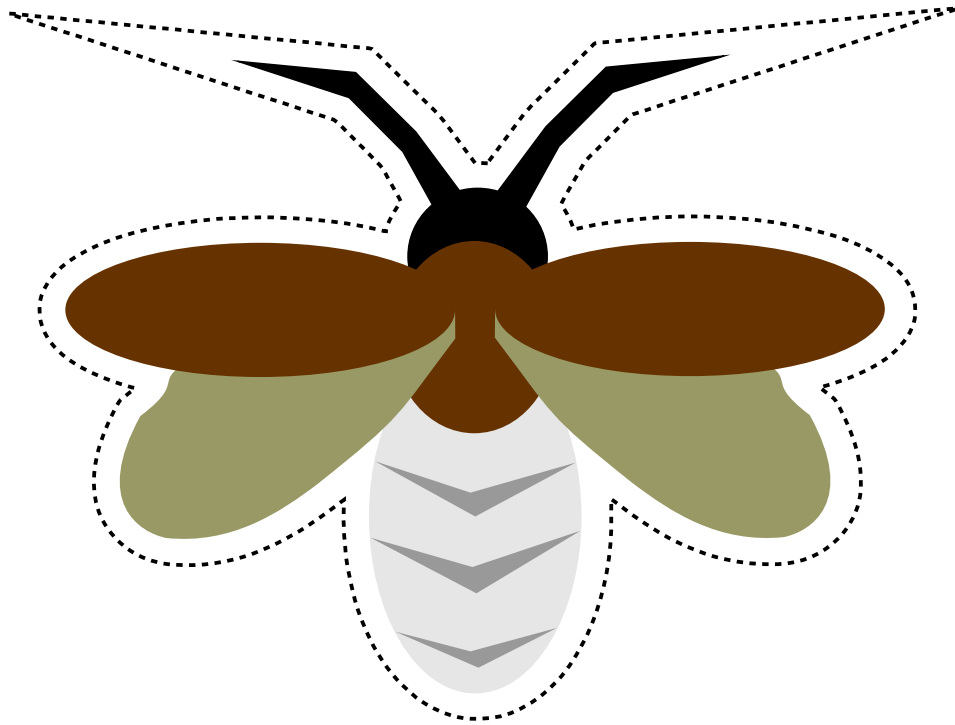


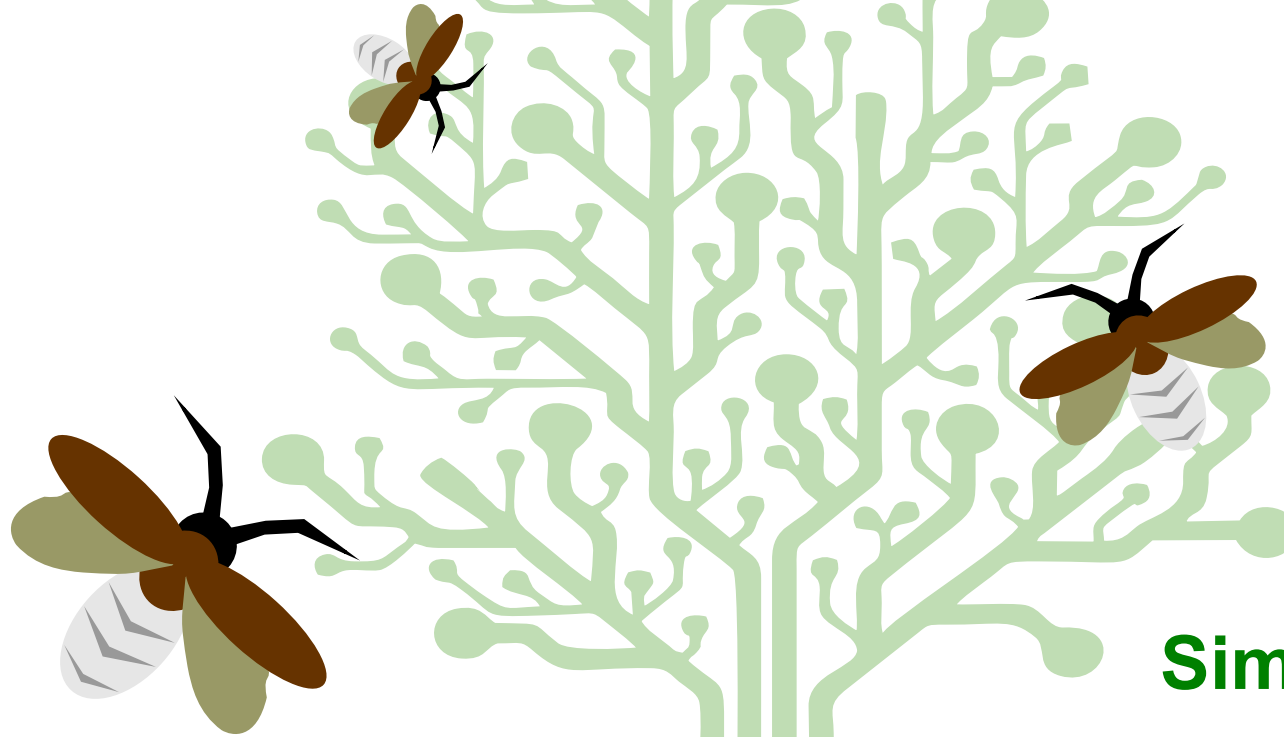**\* print this page separately to cut graphics out later**



**extra\***

\*refer print instruction


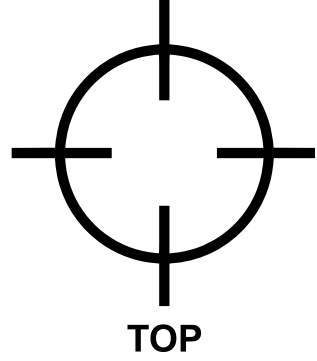

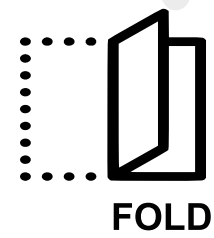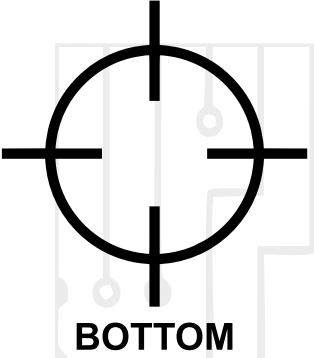
# Simple LED Circuit PAPERTRONIC STEM CARD



LIKE  
COMMENT  
SHARE  
& KEEP LEARNING

[https://www.instructables.com/member/Maker\\_Rahul/](https://www.instructables.com/member/Maker_Rahul/)



# CIRCUIT DIAGRAM

