



Bridge Circuit is balanced when:

$$\frac{R1}{R2} = \frac{R3}{R4}$$