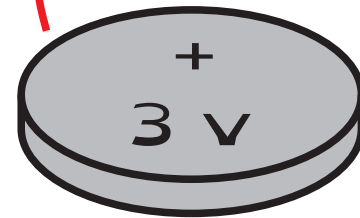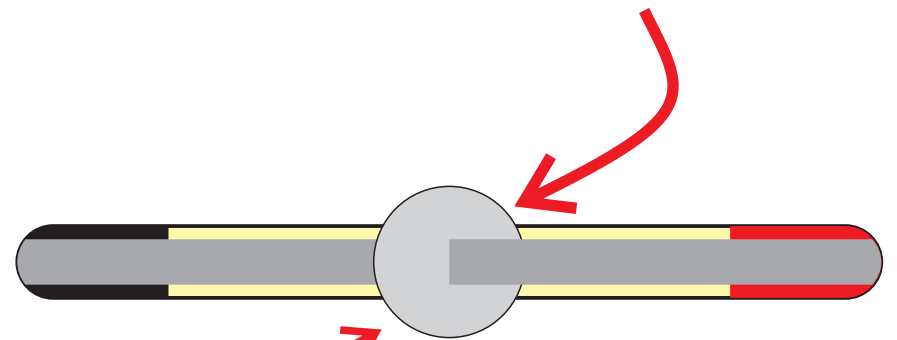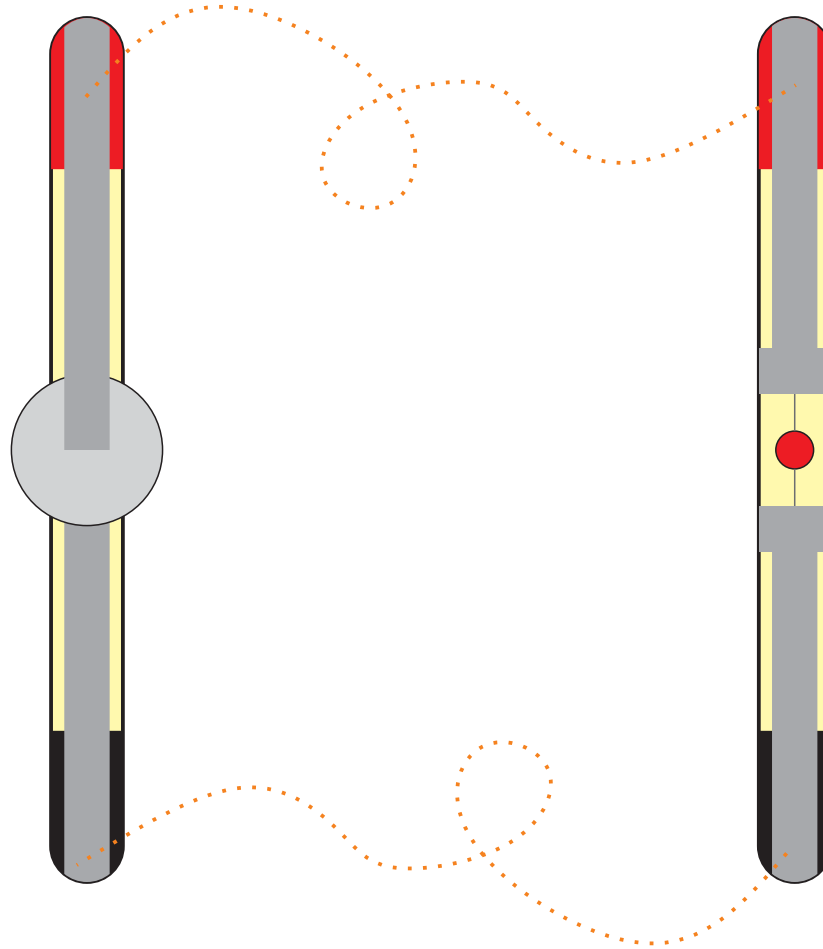**LED**

The **positive** side of the **LED** has a **smaller** piece of electrode and a **longer** leg

The **positive** side of the button battery is **flat and smooth**
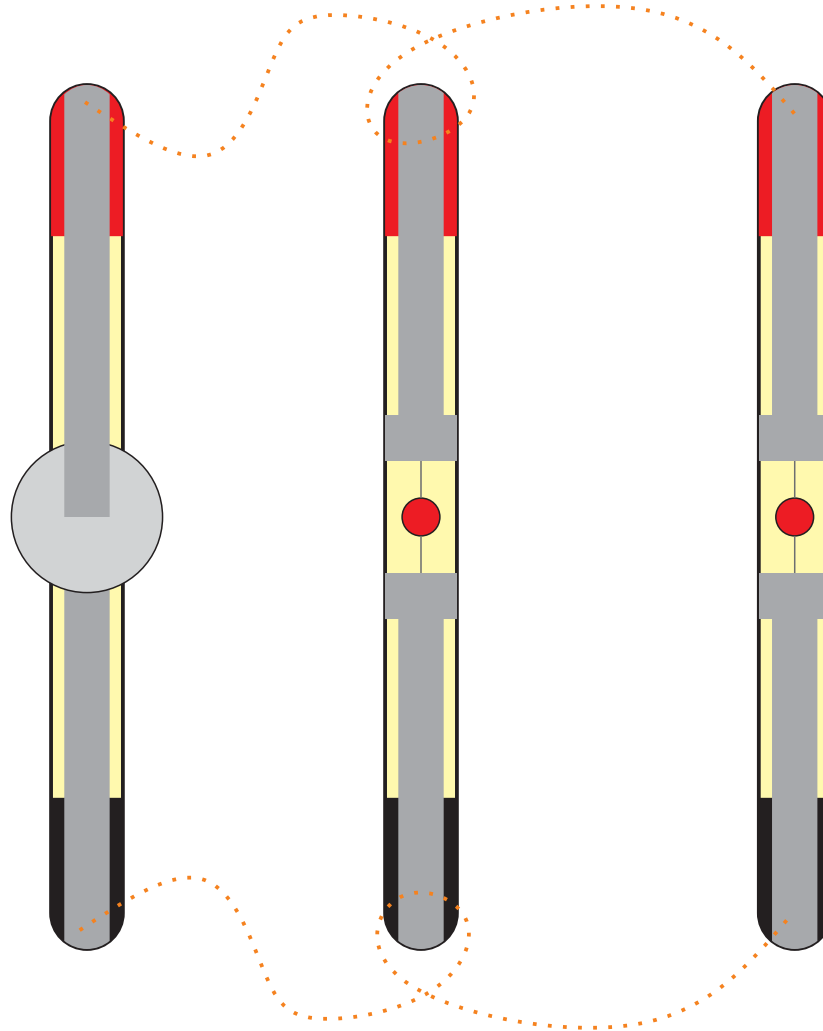
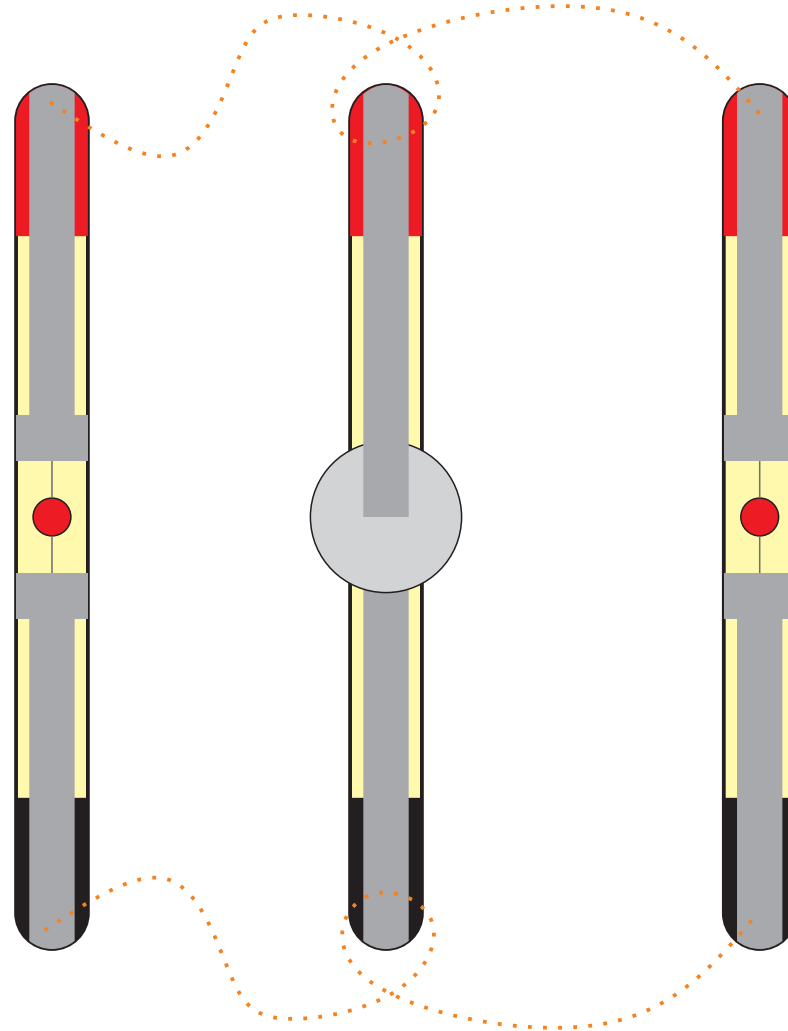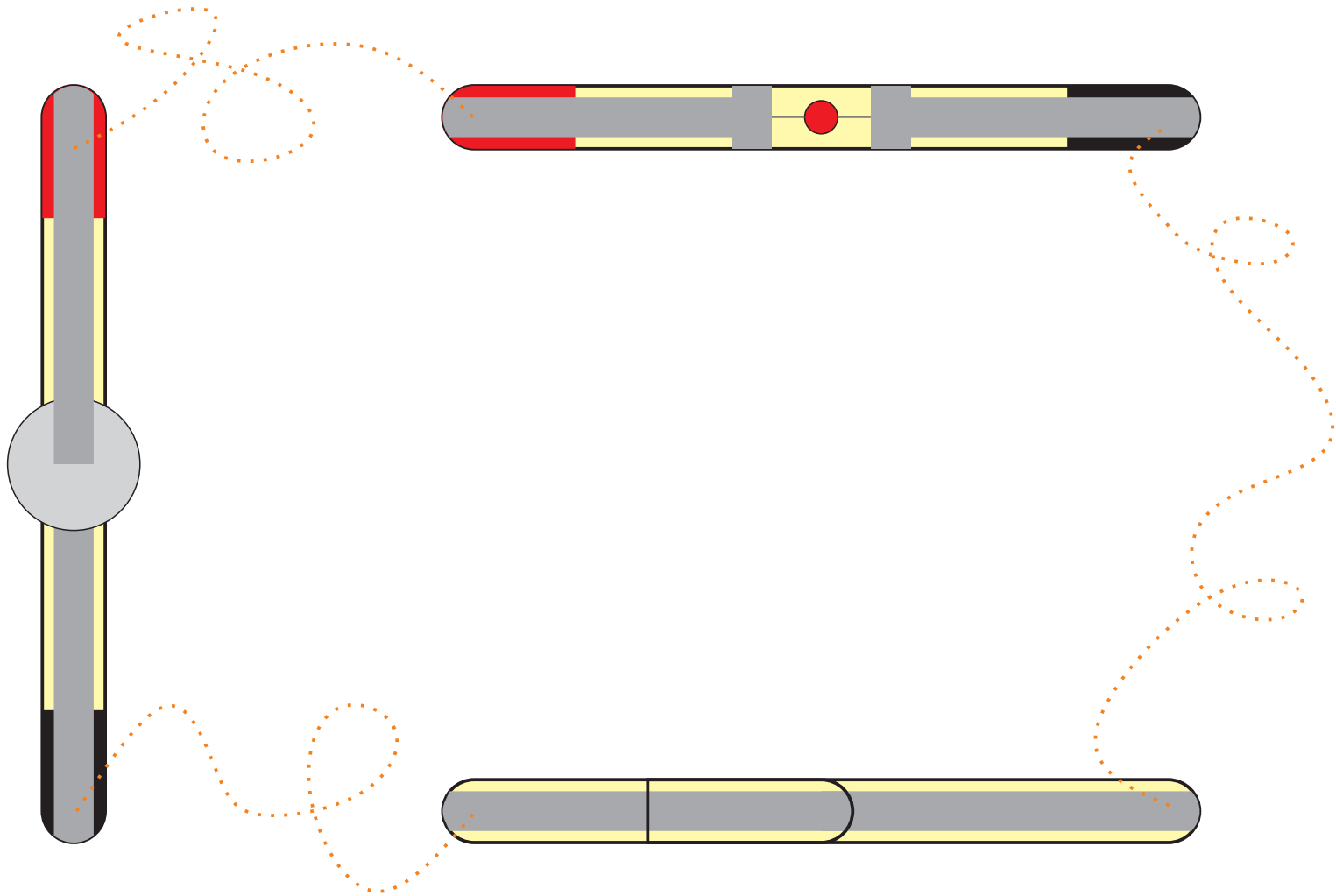**Battery**

+

3 V

1. Make the LED light up!
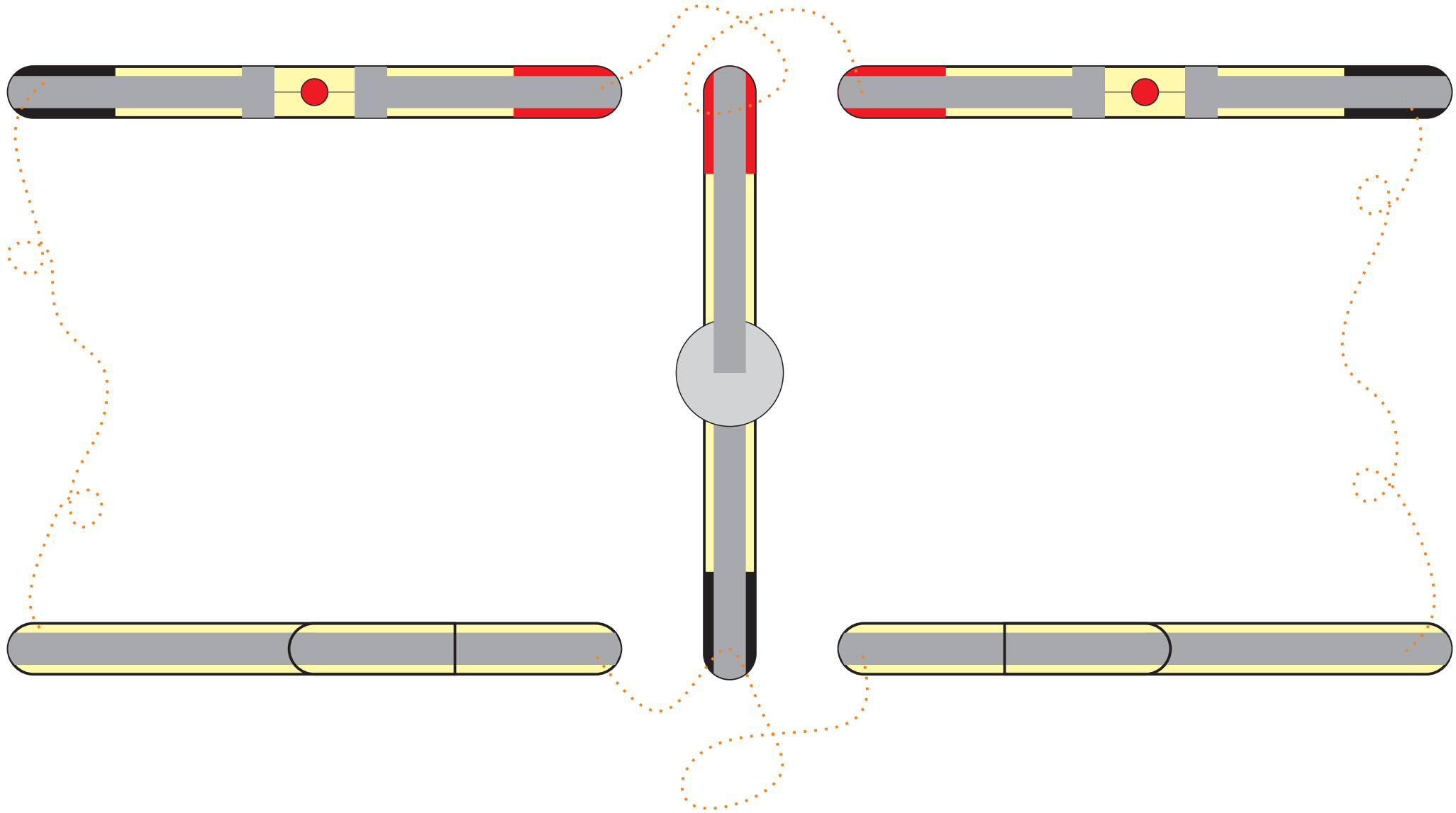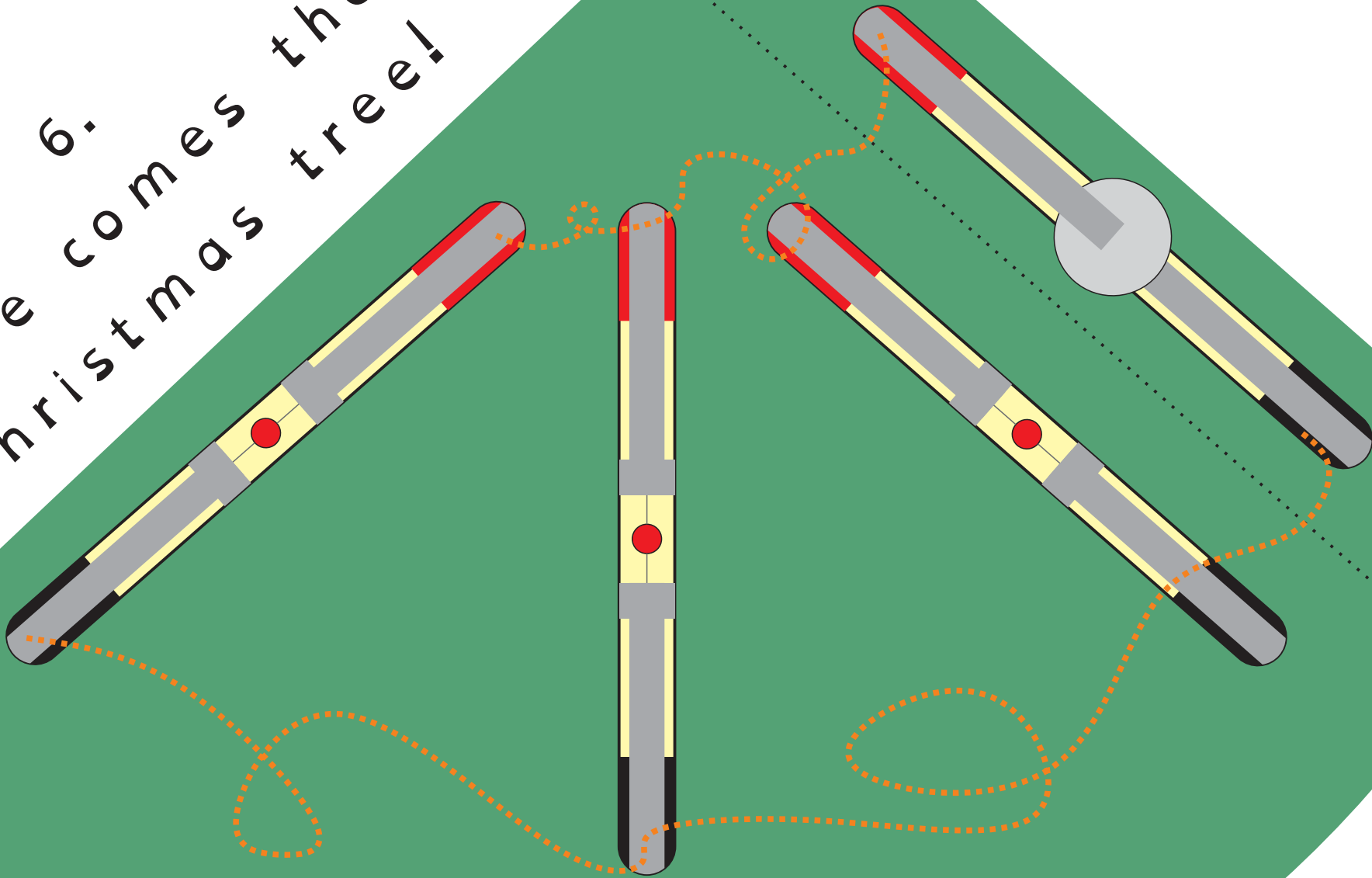
2. Light them all up!

3. Light them all up!

4. Make it blink!

5. Make them blink!

6.

Here comes the Christmas tree!

Design your own
Christmas tree!