



# SANYO Semiconductors DATA SHEET

## CCB (Computer Control Bus) — IC I/F Serial Bus Format

### Overview

This Computer Control Bus (CCB) is a bus format that is designed to ensure that communication in a system configured with a multiple number of ICs is achieved reliably and economically. It is designed for communication between ICs in equipment and not for communication between products requiring long lines.


### Features

The CCB is a single master system, which obviates the need for complex arbitration processing. This reduces the hardware load significantly, enabling the construction of extremely economical systems. Furthermore, many and varied groups of devices including tuners, electronic volumes, digital signal processors for audio application and display drivers are provided to support a broad spectrum of needs. Using software or serial I/O facilities, the CCB can easily interface with many different kinds of controllers so that no special hardware is required.

- CCB is a registered trademark of SANYO Electric Co., Ltd.
- CCB is SANYO Semiconductor's original bus format. All bus addresses are managed by SANYO Semiconductor for this format.

- Any and all SANYO Semiconductor Co.,Ltd. products described or contained herein are, with regard to "standard application", intended for the use as general electronics equipment (home appliances, AV equipment, communication device, office equipment, industrial equipment etc.). The products mentioned herein shall not be intended for use for any "special application" (medical equipment whose purpose is to sustain life, aerospace instrument, nuclear control device, burning appliances, transportation machine, traffic signal system, safety equipment etc.) that shall require extremely high level of reliability and can directly threaten human lives in case of failure or malfunction of the product or may cause harm to human bodies, nor shall they grant any guarantee thereof. If you should intend to use our products for applications outside the standard applications of our customer who is considering such use and/or outside the scope of our intended standard applications, please consult with us prior to the intended use. If there is no consultation or inquiry before the intended use, our customer shall be solely responsible for the use.
- Specifications of any and all SANYO Semiconductor Co.,Ltd. products described or contained herein stipulate the performance, characteristics, and functions of the described products in the independent state, and are not guarantees of the performance, characteristics, and functions of the described products as mounted in the customer's products or equipment. To verify symptoms and states that cannot be evaluated in an independent device, the customer should always evaluate and test devices mounted in the customer's products or equipment.

# CCB (Computer Control Bus)

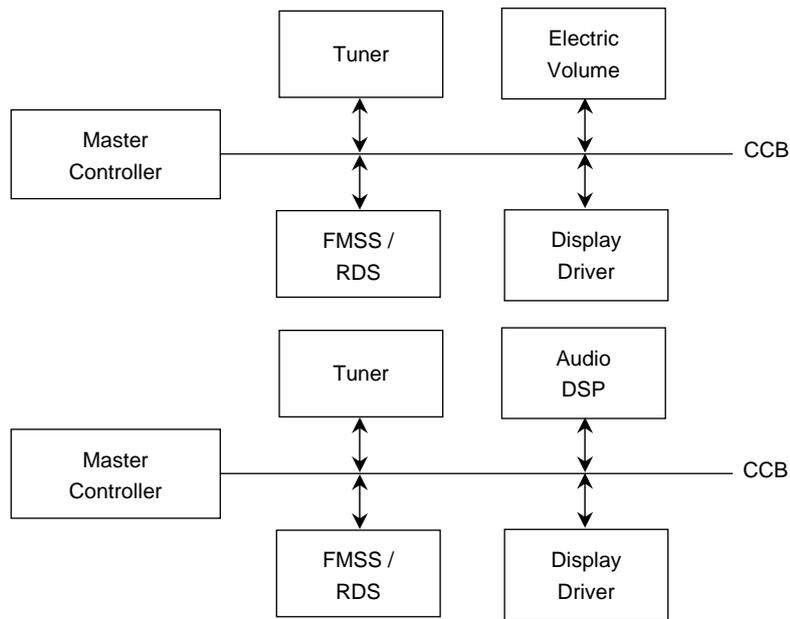


## Configuration of Serial Data Communication

CCB format based communication between the controller and the peripheral ICs can be achieved in two ways: unidirectional communication (one-way communication between the controller and peripheral ICs) or bidirectional communication (two-way communication between the controller and peripheral ICs and two-way communication between the peripheral ICs).

Unidirectional communication is configured with the three lines of the chip enable signal CE, synchronized clock signal CL and input data signal DI, whereas bidirectional communication is configured with the four lines of the chip enable signal CE, synchronized clock signal CL, input data signal DI and output data signal DO. In recent years, ICs with a new means of bidirectional communication, consisting of the three lines of the chip enable signal CE, synchronized clock signal CL and input/output data signal DI/DO, have also been developed.

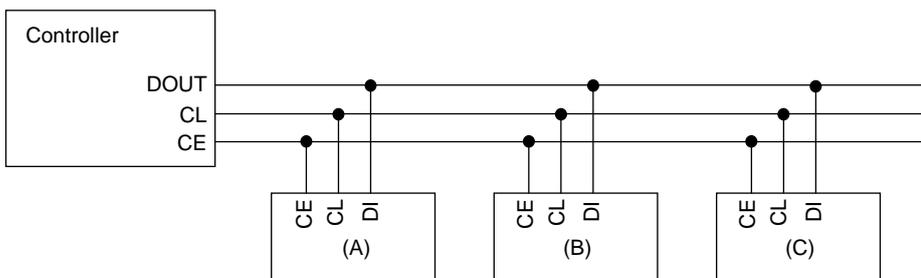
### 1. Unidirectional communication (one-way communication between the controller and peripheral ICs)

Configured with the three lines of the chip enable signal CE, synchronized clock signal CL and input data signal DI



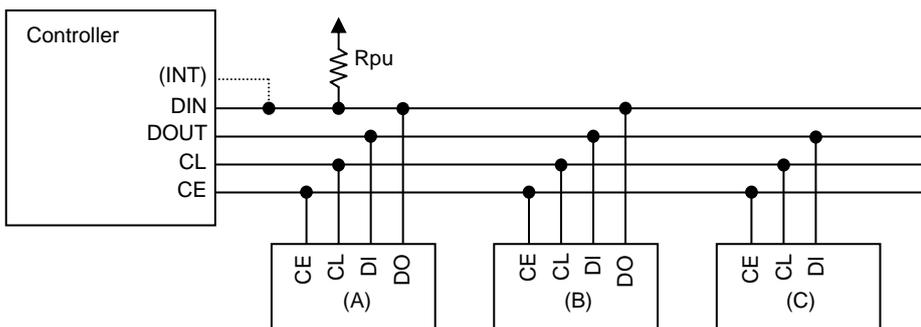
### 2. Bidirectional communication (two-way communication between the controller and peripheral ICs)

<2-1> Configured with the four lines of the chip enable signal CE, synchronized clock signal CL, input data signal DI and output data signal DO


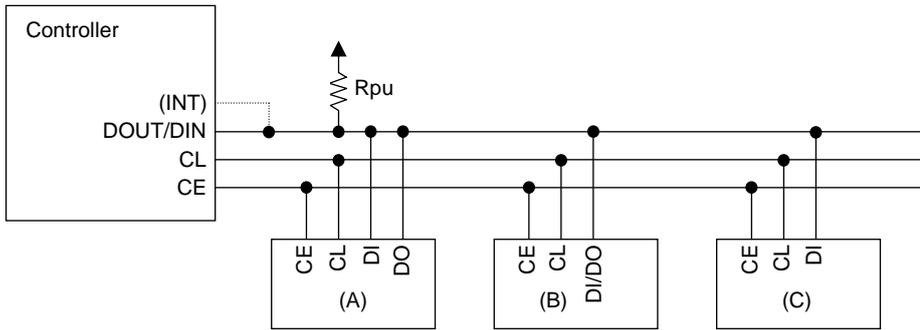
## CCB (Computer Control Bus)

<2-2> Configured with the three lines of the chip enable signal CE, synchronized clock signal CL and input/output data signal DI/DO (This means of bidirectional communication is new for the CCB, and ICs featuring this function must be employed in order to use this communication method.)



[Note] Rpu: Pull-up resistor

(INT): Input port for detecting data read request signal

### Serial Data Communication Format


Under the CCB format, when data is to be sent from the controller to the peripheral ICs, it is sent by the following series of operations. The controller transfers the CCB addresses B0 to B3 and A0 to A3 while the chip enable signal CE is low. After all the addresses have been transferred, the CE signal level is switched from low to high, and while this signal is high, the data DI0 to DI<sub>n</sub> (input data) required by the peripheral ICs is transferred. The CE signal level is then switched from high to low. In addition, the CCB addresses and input data to be sent from the controller are imported into the peripheral ICs by the rising edge of the CL signal.

On the other hand, when data is to be received by the controller from the peripheral ICs, it is received by the following series of operations. The controller transfers the CCB addresses B0 to B3 and A0 to A3 while the chip enable signal CE is low. After all the addresses have been transferred, the CE signal level is switched from low to high, and while this signal is high, the data DO0 to DO<sub>m</sub> (output data) is read from the peripheral ICs. CE signal level is then switched from high to low. In addition, since the CCB addresses to be sent from the controller are imported into the peripheral ICs by the rising edge of the CL signal, and the output data to be received by the controller is output from the peripheral ICs in synchronization with the falling edge of the CL signal, the controller can import the output data DO0 to DO<sub>m</sub> at the rising edge of the CL signal.

As a basic rule, the CCB addresses have a bit width of 8 bits, and the data has a bit width that is a multiple of 8 ( $8 \times a$  bit width where "a" is a natural number). However, there are 4-bit CCB address groups among the CCB address groups so, in this case, dummy data must be added to the CCB addresses B0 to B3.


#### 1. Unidirectional communication format (consisting of the 3 lines of CE, CL, and DI)

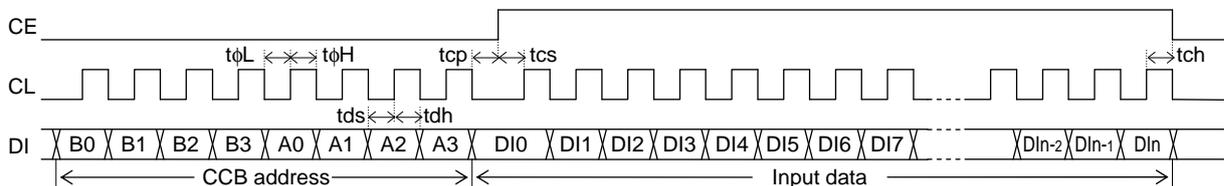(1) When communication is stopped with CL at the low level



# CCB (Computer Control Bus)

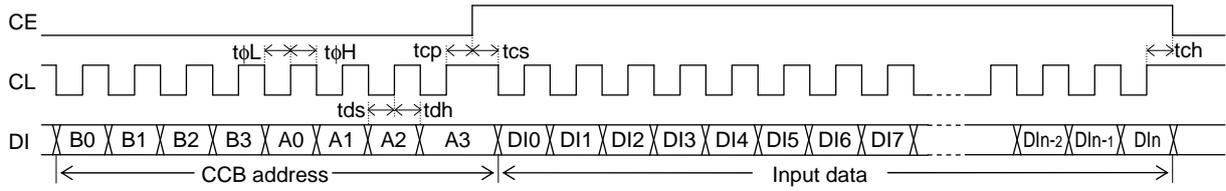(2) When communication is stopped with CL at the high level



[Note]

tds: Data setup time

tdh: Data hold time

tcp: CE wait time

tcs: CE setup time

tch: CE hold time

$t_{\phi H}$ : High level clock pulse width


$t_{\phi L}$ : Low level clock pulse width

## 2. Bidirectional communication format


<2-1> Bidirectional communication format (consisting of the 4 lines of CE, CL, DI, and DO)

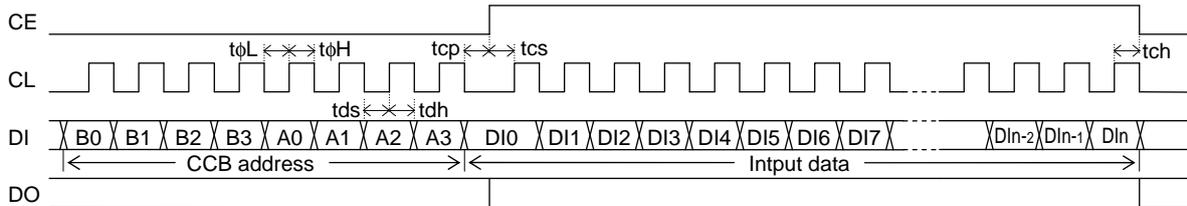(1) When communication is stopped with CL at the low level

① When the controller sends the data to the peripheral ICs (serial data input)




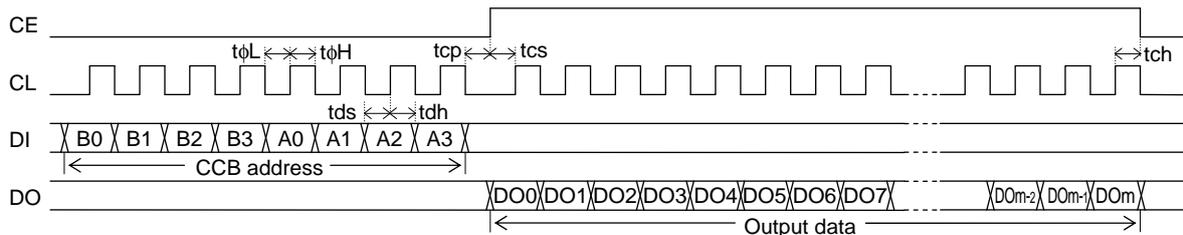② When the controller receives the data from the peripheral ICs (serial data output)



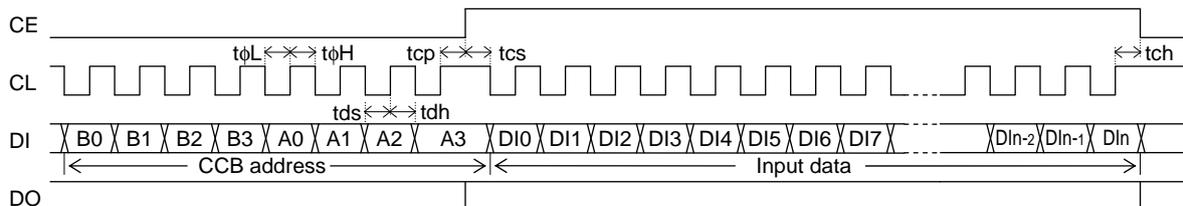
(2) When communication is stopped with CL at the high level

① When the controller sends the data to the peripheral ICs (serial data input)


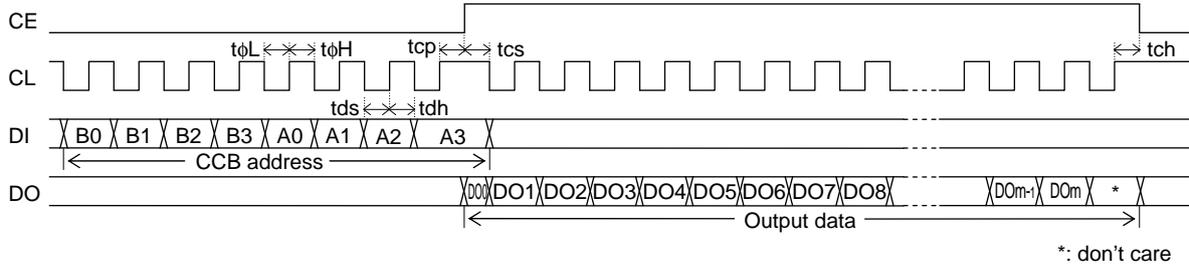
# CCB (Computer Control Bus)

② When the controller receives the data from the peripheral ICs (serial data output)




[Note] The output data DO0 to DOm is shifted by 1 bit between ① when communication is stopped with CL at the low level and ② when communication is stopped with CL at the high level, so that use of the output data DO0 is not recommended. Furthermore, when using output data DO0, the status of the DO signal immediately after the CE signal level has changed from low to high must be detected.

## <2-2> Bidirectional communication format (consisting of the 3 lines of CE, CL, and DI/DO)


(This means of bidirectional communication is new for the CCB, and devices featuring this function must be employed in order to use this communication method.)

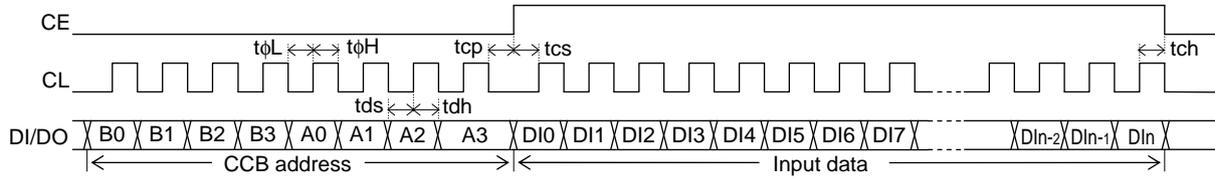(1) When communication is stopped with CL at the low level

① When the controller sends the data to the peripheral ICs (serial data input)




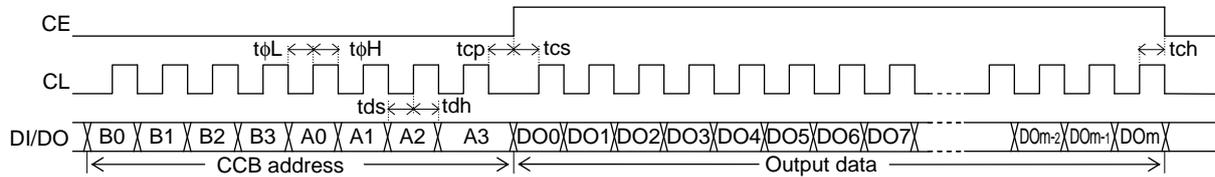② When the controller receives the data from the peripheral ICs (serial data output)




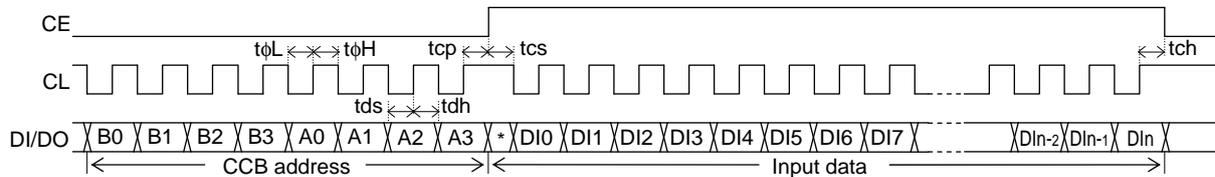(2) When communication is stopped with CL at the high level

① When the controller sends the data to the peripheral ICs (serial data input)



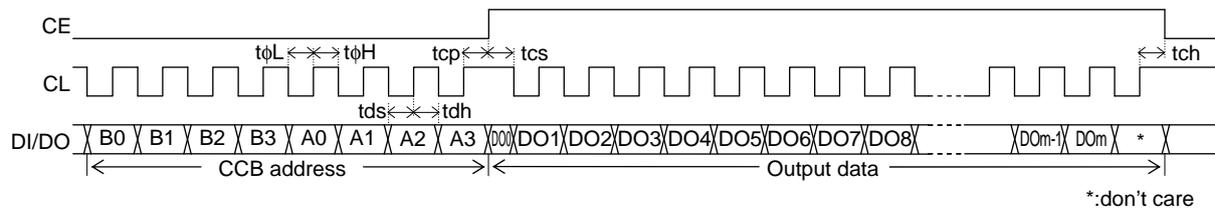② When the controller receives the data from the peripheral ICs (serial data output)




[Note] The output data DO0 to DOm is shifted by 1 bit between ① when communication is stopped with CL at the low level and ② when communication is stopped with CL at the high level so that use of the output data DO0 is not recommended. Furthermore, when using output data DO0, the status of the DI/DO signal immediately after the CE signal level has changed from low to high must be detected.

# CCB (Computer Control Bus)
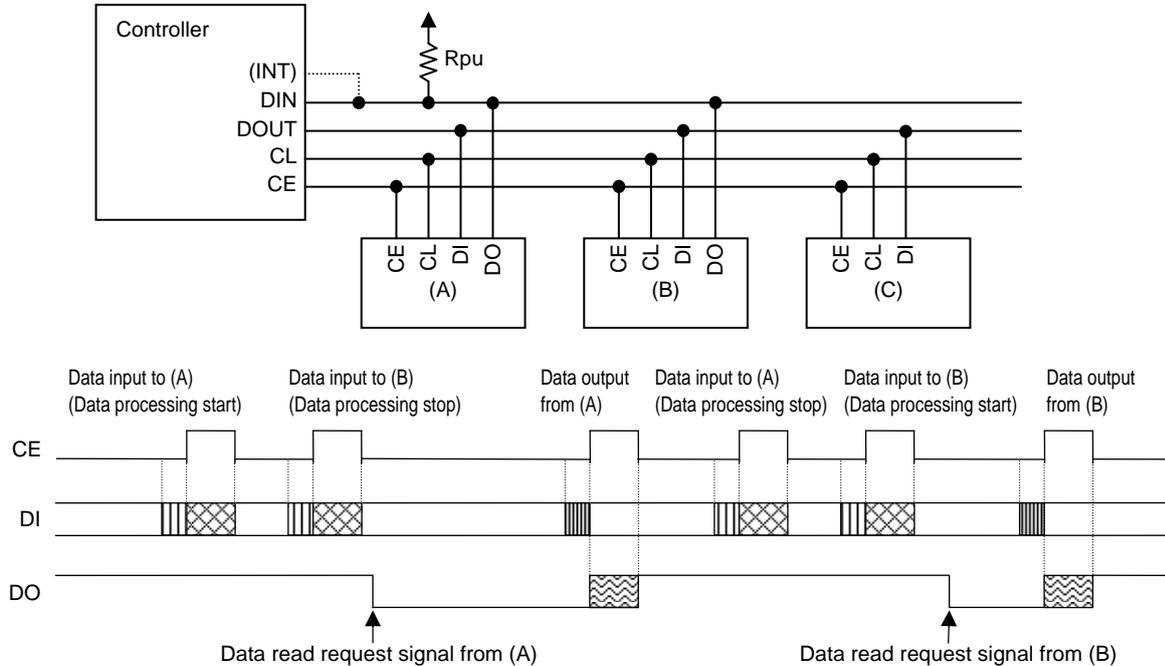
## Concerning the Data Read Request Signal and Serial Data Communication


Also provided with the CCB format is a function that passes the data read request signal along the output data signal DO line and outputs it to the controller for cases in which data that has been processed by the peripheral ICs is to be output to the controller, or where the peripheral ICs request that the serial data be sent from the controller, for instance. In addition, when serial data communication is not performed between the controller and peripheral ICs (when the chip enable signal CE level is low), the data read request signal is output by setting the output data signal DO to the low level, and when the controller detects this data read request signal, it proceeds to read the data as shown below for the peripheral ICs.

<1> Bidirectional communication format (consisting of the 4 lines of CE, CL, DI, and DO)



<2> Bidirectional communication format (consisting of the 3 lines of CE, CL, and DI/DO)

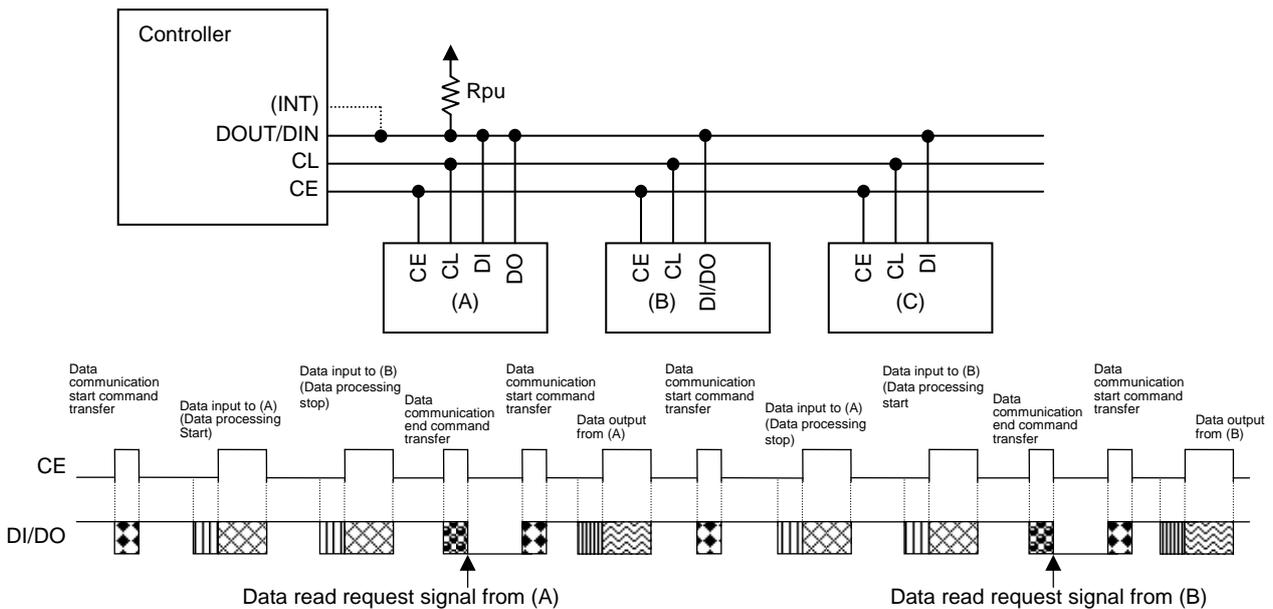(This means of bidirectional communication is new for the CCB, and ICs featuring this function must be employed in order to use this communication method.)




[Note] When serial data communication is to be performed, the data communication start command must be transferred. When the data read request signal (DO = low) is to be detected, the data communication end command must be transferred. For further details on the data communication start and end commands, refer to the individual specification document of each device.

# CCB (Computer Control Bus)

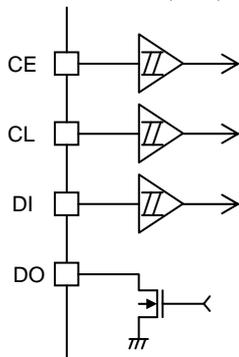
## Concerning the Interface Pins Connected to the Controller

The chip enable signal input pin CE, synchronized clock signal input pin CL and input data signal input pin DI of the peripheral ICs are input pins that are configured using schmitt circuits, among others. The output data signal output pin DO is an output pin that is configured with an open-drain N-channel transistor, for instance, and a pull-up resistor is required. The electrical characteristics of these pins are as shown below. (For further details on the electrical characteristics of these pins, refer to the individual catalog and delivery specification documents of each device.)

<1> Equivalent circuits of CE, CL, DI and DO pins


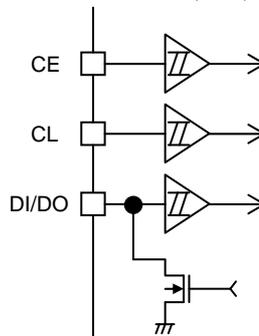
<2> Equivalent circuits of CE, CL, and DI/DO pins



### 1. Example of electrical characteristics of CE, CL and DI input pins

[Example 1]  $V_{IN} = -0.3$  to  $+4.2V$  or  $V_{IN} = -0.3$  to  $+6.5V$

In this example, the IC can apply a voltage to the CE, CL and DI pins regardless of supply voltage  $V_{DD}$ . Even when no power is supplied to the IC, voltages can be applied to the CE, CL and DI pins.

However, care is required since the maximum voltage that can be applied differs from one IC to another. If the specifications give  $V_{IN} = -0.3$  to  $+4.2V$ , for instance, a 3.3V voltage can be applied regardless of supply voltage  $V_{DD}$ , but a 5V voltage cannot be applied. (If the specifications give  $V_{IN} = -0.3$  to  $+6.5V$ , a 5V voltage can be applied regardless of supply voltage  $V_{DD}$ .)

[Example 2]  $V_{IN} = -0.3$  to  $+6.5V$  (provided that supply voltage  $V_{DD} = 3.0$  to  $3.6V$ )

In this example, when a 3.0 to 3.6V voltage is supplied to supply voltage  $V_{DD}$ , a voltage can be applied to the CE, CL and DI pins regardless of the supply voltage  $V_{DD}$ . In other words, if a 3.0 to 3.6V voltage is being supplied to supply voltage  $V_{DD}$  of the IC, it is possible to apply a 3.3V or 5V voltage to the CE, CL and DI pins.

[Example 3]  $V_{IN} = -0.3$  to  $V_{DD} + 0.3V$

In this example, the IC cannot apply a voltage in excess of supply voltage  $V_{DD}$  to the CE, CL and DI pins, and a voltage equivalent to supply voltage  $V_{DD}$  or less can be supplied to these pins while power is being supplied to the IC. If no power is supplied to the device, supply voltage  $V_{DD}$  is normally the same as  $V_{SS}$  (GND) so that the CE, CL and DI pins must have the same potential as  $V_{SS}$  (GND).

### 2. Example of electrical characteristics of DO output pin

[Example 1]  $V_{OUT} = -0.3$  to  $+4.2V$  or  $V_{OUT} = -0.3$  to  $+6.5V$

In this example, the IC can apply a pull-up voltage to the DO pin regardless of supply voltage  $V_{DD}$ . Even when no power is being supplied to the IC, a pull-up voltage can be applied to the DO pin.

However, care is required since the maximum pull-up voltage that can be applied differs from one IC to another.

If the specifications give  $V_{OUT} = -0.3$  to  $+4.2V$ , for instance, a 3.3V pull-up voltage can be applied regardless of supply voltage  $V_{DD}$ , but a 5V voltage cannot be applied. (If the specifications give  $V_{OUT} = -0.3$  to  $+6.5V$ , a 5V pull-up voltage can be applied regardless of supply voltage  $V_{DD}$ .)

[Example 2]  $V_{OUT} = -0.3$  to  $V_{DD} + 0.3V$

In this example, the IC cannot apply a pull-up voltage in excess of supply voltage  $V_{DD}$  to the DO pin, and a pull-up voltage equivalent to supply voltage  $V_{DD}$  or less can be applied to this pin while power is being supplied to the IC. If no power is supplied to the IC, the pull-up voltage of the DO pin must be set to off or steps must be taken to isolate the DO pin from the pull-up power supply, for instance.

# CCB (Computer Control Bus)

## CCB Address Group

### 1. 8-bit address group

CCB address								Hex display	Device name (IC name)		
Binary display											
LSB	B0	B1	B2	B3	A0	A1	MSB			A2	A3
	0	0	0	0	0	0	0	0	0	00	Used for data communication start and end commands
	0	0	0	0	1	0	0	0	0	10	
	1	0	0	0	1	0	0	0	0	11	
	↓								↓	↓	
	1	1	1	1	1	0	0	0	0	1F	
	0	0	0	0	0	1	0	0	0	20	
	1	0	0	0	0	1	0	0	0	21	
	↓								↓	↓	
	0	0	0	1	0	1	0	0	0	28	LV23xxx series, LV25xxx series (Tuner)
	1	0	0	1	0	1	0	0	0	29	LV23xxx series, LV25xxx series (Tuner)
	0	1	0	1	0	1	0	0	0	2A	LV23xxx series, LV25xxx series (Tuner)
	↓								↓	↓	
	1	1	1	1	0	1	0	0	0	2F	
	0	0	0	0	1	1	0	0	0	30	
	1	0	0	0	1	1	0	0	0	31	
	↓								↓	↓	
	1	1	1	1	1	1	0	0	0	3F	
	0	0	0	0	0	0	1	0	0	40	LC758xx series (LCD display driver)
	1	0	0	0	0	0	1	0	0	41	LC758xx series (LCD display driver)
	0	1	0	0	0	0	1	0	0	42	LC758xx series (LCD display driver)
	1	1	0	0	0	0	1	0	0	43	LC758xx series (LCD display driver)
	↓								↓	↓	
	1	1	1	1	0	0	1	0	0	4F	LC758xx series (LCD display driver)
	0	0	0	0	1	0	1	0	0	50	
	1	0	0	0	1	0	1	0	0	51	
	↓								↓	↓	
	1	1	1	1	1	0	1	0	0	5F	
	0	0	0	0	0	1	1	0	0	60	
	1	0	0	0	0	1	1	0	0	61	
	0	1	0	0	0	1	1	0	0	62	LC75700 (Key scan IC)
	1	1	0	0	0	1	1	0	0	63	LC75700 (Key scan IC)
	↓								↓	↓	
	0	1	0	1	0	1	1	0	0	6A	LC72720, LC72722 (RDS)
	1	1	0	1	0	1	1	0	0	6B	LC72720, LC72722 (RDS)
	0	0	1	1	0	1	1	0	0	6C	LC72720, LC72722 (RDS)
	↓								↓	↓	
	1	1	1	1	0	1	1	0	0	6F	
	0	0	0	0	1	1	1	0	0	70	
	1	0	0	0	1	1	1	0	0	71	
	↓								↓	↓	
	1	1	1	1	1	1	1	0	0	7F	
	0	0	0	0	0	0	0	1	0	80	
	1	0	0	0	0	0	0	1	0	81	LC754x series (Electronic volume)
	0	1	0	0	0	0	0	1	0	82	LC753x series (Electronic volume)
	↓								↓	↓	

Continued on next page.

## CCB (Computer Control Bus)

Continued from next page

CCB address								Hex display	Device name (IC name)		
Binary display											
LSB	B0	B1	B2	B3	A0	A1	A2			A3	MSB
	0	1	1	1	0	0	0	0	1	8E	LC757xx series (VFD display driver)
	1	1	1	1	0	0	0	0	1	8F	LC757xx series (VFD display driver)
	0	0	0	0	1	0	0	0	1	90	
	1	0	0	0	1	0	0	0	1	91	
↓								↓	↓		
	1	1	1	1	1	0	0	0	1	9F	
	0	0	0	0	0	1	0	0	1	A0	
	1	0	0	0	0	1	0	0	1	A1	
	0	1	0	0	0	1	0	0	1	A2	LC758xx series (LCD display driver)
↓								↓	↓		
	1	1	1	1	0	1	0	0	1	AF	
	0	0	0	0	1	1	0	0	1	B0	
	1	0	0	0	1	1	0	0	1	B1	
↓								↓	↓		
	1	1	1	1	1	1	0	0	1	BF	
	0	0	0	0	0	0	1	0	1	C0	
	1	0	0	0	0	0	1	0	1	C1	
↓								↓	↓		
	1	1	1	1	0	0	1	0	1	CF	
	0	0	0	0	1	0	1	0	1	D0	
	1	0	0	0	1	0	1	0	1	D1	LC7501x series,LC7502x series (Audio DSP)
	0	1	0	0	1	0	1	0	1	D2	LC7501x series,LC7502x series (Audio DSP)
↓								↓	↓		
	1	1	1	0	1	0	1	0	1	D7	LC7505x series (Lip-sync surround)
	0	0	0	1	1	0	1	0	1	D8	LC7505x series (Lip-sync surround)
↓								↓	↓		
	1	1	1	1	1	0	1	0	1	DF	
	0	0	0	0	0	1	1	0	1	E0	
	1	0	0	0	0	1	1	0	1	E1	
↓								↓	↓		
	0	0	0	1	0	1	1	0	1	E8	LC8905x series (DIR/DIT)
	1	0	0	1	0	1	1	0	1	E9	LC8905x series (DIR/DIT)
	0	1	0	1	0	1	1	0	1	EA	LC8905x series (DIR/DIT)
	1	1	0	1	0	1	1	0	1	EB	LC8905x series (DIR/DIT)
	0	0	1	1	0	1	1	0	1	EC	LC8905x series (DIR/DIT)
	1	0	1	1	0	1	1	0	1	ED	LC8905x series (DIR/DIT)
↓								↓	↓		
	1	1	1	1	0	1	1	0	1	EF	
	0	0	0	0	1	1	1	0	1	F0	
	1	0	0	0	1	1	1	0	1	F1	
↓								↓	↓		
	0	1	0	1	1	1	1	0	1	FA	LC7270x series (FMSS)
	1	1	0	1	1	1	1	0	1	FB	LC7270x series (FMSS)
	0	0	1	1	1	1	1	0	1	FC	LC7270x series (FMSS)
	1	0	1	1	1	1	1	0	1	FD	LC7270x series (FMSS)
↓								↓	↓		
	1	1	1	1	1	1	1	0	1	FF	

## CCB (Computer Control Bus)

### 2. 4-bit address group

CCB address								Hex display	Device name (IC name)
Binary display									
LSB				MSB					
B0	B1	B2	B3	A0	A1	A2	A3		
X	X	X	X	1	0	0	0	1	
X	X	X	X	0	1	0	0	2	
X	X	X	X	1	1	0	0	3	
X	X	X	X	0	0	1	0	4	LC7573F (VFD display driver)
X	X	X	X	1	0	1	0	5	LC7574F (VFD display driver)
↓								↓	↓
X	X	X	X	0	1	0	1	A	LC78211 (Function switch)
X	X	X	X	1	1	0	1	B	LC78211 (Function switch)
X	X	X	X	0	0	1	1	C	LC78212 (Function switch)
X	X	X	X	1	0	1	1	D	LC78212 (Function switch)
X	X	X	X	0	1	1	1	E	LC78213 (Function switch)
X	X	X	X	1	1	1	1	F	LC78213 (Function switch)

[Note] For serial data communication in 8-bit units, dummy data must be added to CCB addresses B0 to B3.

For serial data communication in 4-bit units, the data in CCB addresses B0 to B3 need not be transferred, but if ICs in the 8-bit address group and ICs in the 4-bit address group are to be connected on the same bus line, dummy data must be added to CCB addresses B0 to B3.

- SANYO Semiconductor Co.,Ltd. assumes no responsibility for equipment failures that result from using products at values that exceed, even momentarily, rated values (such as maximum ratings, operating condition ranges, or other parameters) listed in products specifications of any and all SANYO Semiconductor Co.,Ltd. products described or contained herein.
- SANYO Semiconductor Co.,Ltd. strives to supply high-quality high-reliability products, however, any and all semiconductor products fail or malfunction with some probability. It is possible that these probabilistic failures or malfunction could give rise to accidents or events that could endanger human lives, trouble that could give rise to smoke or fire, or accidents that could cause damage to other property. When designing equipment, adopt safety measures so that these kinds of accidents or events cannot occur. Such measures include but are not limited to protective circuits and error prevention circuits for safe design, redundant design, and structural design.
- In the event that any or all SANYO Semiconductor Co.,Ltd. products described or contained herein are controlled under any of applicable local export control laws and regulations, such products may require the export license from the authorities concerned in accordance with the above law.
- No part of this publication may be reproduced or transmitted in any form or by any means, electronic or mechanical, including photocopying and recording, or any information storage or retrieval system, or otherwise, without the prior written consent of SANYO Semiconductor Co.,Ltd.
- Any and all information described or contained herein are subject to change without notice due to product/technology improvement, etc. When designing equipment, refer to the "Delivery Specification" for the SANYO Semiconductor Co.,Ltd. product that you intend to use.
- Information (including circuit diagrams and circuit parameters) herein is for example only; it is not guaranteed for volume production.
- Upon using the technical information or products described herein, neither warranty nor license shall be granted with regard to intellectual property rights or any other rights of SANYO Semiconductor Co.,Ltd. or any third party. SANYO Semiconductor Co.,Ltd. shall not be liable for any claim or suits with regard to a third party's intellectual property rights which has resulted from the use of the technical information and products mentioned above.

This catalog provides information as of October, 2008. Specifications and information herein are subject to change without notice.